COMMERCIAL OSCILLOSCOPES AND RELATED EQUIPMENT

HICKOK MODEL 195

Frequency Response Vertical Amplifier 10 cps to 50 kc Horizontal Amplifier 10 cps to 50 kc

DEFLECTION FACTORS

Vertical-Deflection Plates 0.05 rms volts/inch Vertical Amplifier 15 rms volts/inch Horizontal Amplifier 0.3 rms volts/inch Horizontal-Deflection Plates 30 rms volts/inch

LINE RATING 105-125 volts, 50-70 cps

TUBE COMPLEMENT

Type	Function
6SJ7 (V1)	Horizontal Amplifier
884 (V2)	Sweep Circuit Oscillator
6AC7 (V3)	Vertical Amplifier
6X5GT (V4)	Low-Voltage Rectifier
5Y3GT (V5)	High-Voltage Rectifier
5UP1	Cathode-Ray Tube

The schematic circuit diagram of Model 195 is shown in Fig. 22-32. One feature of this otherwise conventional instrument is the use of a phasing control, R3, to apply a voltage derived from the V4 plate circuit to C8 through the S1 horizontal selector switch. C11, C9, R8, R4, C6, and R3 make up the phasing network. There is a voltage division of the 350-volt, 60-cycle signal, between C11 and C9. The signal voltage across C9 is applied to R12 through S1, C8, and R8. R3 affects the amplitude and phase by changing the circuit impedance.

HICKOK MODEL 195B

FREQUENCY RESPONSE

Vertical Amplifier 30 cps to 1,000 kc Horizontal Amplifier 10 cps to 50 kc Sweep Circuit 10 cps to 25 kc

Deflection Factors

Vertical Amplifier 0.03 rms volts/inch Vertical-Deflection Plates 15 rms volts/inch Horizontal Amplifier 0.3 rms volts/inch Horizontal-Deflection Plates 30 rms volts/inch

Line Rating 105-125 volts, 50-70 cps

TUBE COMPLEMENT

Type	Function
6SJ7 (V1)	Horizontal Amplifier
884 (V2)	Sweep Circuit Öscillator
6SN7 (V3)	Vertical Cathode-Follower Input Amplifier
6AC7 (V4)	Vertical Amplifier
6X5GT (V5)	Low-Voltage Rectifier
5Y3GT (V6)	High-Voltage Rectifier
5UP1	Cathode-Ray Tube

The schematic circuit diagram of Model 195B is shown in Fig. 22-33. This oscilloscope provides for external Z-axis or intensity grid modulation of the cathode-ray tube. A signal may be fed to pin 2 of the cathode-ray tube through C31 and S5, using either external or internal modulation. The horizontal sweep and remaining circuits are very much like those of Hickok Model 195. However, the phasing control and filter circuits are a little different. Two filters, C32 and C33, are used instead of four filters. The phasing voltage is derived from the transformer primary rather than from the high-voltage secondary.

HICKOK MODEL 305

Frequency Response

Vertical Amplifier 30 cps to 1 Mc Horizontal Amplifier 10 cps to 50 kc Sweep Circuit 10 cps to 25 kc F.M. Oscillator 0-30 kc, and 0-450 kc

Line Rating 115 volts, 60 cps

The tube complement and tube functions of Model 305 are given in the schematic diagram, Fig. 22-34. This oscilloscope is similar to Hickok Model RFO-5. It should be noted, however, that Model RFO-5 uses 1,000 kc and 23 Mc for the r-f oscillator, while Model 305 uses 1,000 kc and 50 Mc. The use of the V6 cathode-follower also permits the employment of a low-impedance vertical gain control R50 of 10,000 ohms in place of the high-impedance control R114 in Model RFO-5. The low-impedance control has less frequency discrimination and is, therefore, an improvement. The signal tracer jack J1 is in the low-impedance cathode circuit of V5, rather than in the high Z-plate circuit of V103 in the RFO-5. A connection to it, therefore, is a less critical matter. High-frequency compensation in the form of L2 and L3 is used to give a wideband characteristic in the vertical-amplifier stage.

HICKOK MODEL 505A

FREQUENCY RESPONSE

Vertical Amplifier 30 cps to 1 Mc Horizontal Amplifier 10 cps to 50 kc Sweep Circuit 10 cps to 25 kc

DEFLECTION FACTORS

Vertical Amplifier 0.08 rms volts/inch Vertical-Deflection Plates 15 rms volts/inch Horizontal Amplifier 0.13 rms volts/inch Horizontal-Deflection Plates 30 rms volts/inch

LINE RATING 105-125 volts, 50-70 cps

The tube complement and its functions for Model 505A are shown in the schematic circuit diagram, Fig. 22-35. Model 505A is very similar to the 305 electrically.

JACKSON MODEL CRO-1

FREQUENCY RESPONSE

Vertical Amplifier—Wideband 20 cps to 4½ Mc Vertical Amplifier—High Sensitivity 20 cps to 100 kc Horizontal Amplifier 20 cps to 150 kc Sweep Circuit 20 cps to 50 kc

Deflection Factors


Vertical Amplifier—Wideband 0.25 rms volts/inch Vertical Amplifier—High Sensitivity 0.018 rms volts/inch Vertical-Deflection Plates 12 rms volts/inch Horizontal Amplifier 0.55 rms volts/inch Horizontal-Deflection Plates 15 rms volts/inch

Line Rating 100-125 volts, 50-60 cps

TUBE COMPLEMENT

Type	Function
5Y3 (V1, V2)	Rectifiers
6J6 (V3, V4, V5)	Amplifiers
6J6 (V6)	Sweep Oscillator
6C4 (V7, V8)	Cathode Followers
5UP1 (V9)	Cathode-Ray Tube

The schematic circuit diagram for Model CRO-1 is shown in Fig 22-36. The vertical amplifiers are operated in a high-gain circuit to provide a sensitivity of 0.018 volts per inch in the high-sensitivity position. They are switched to video-type amplifiers in the wideband position and provide 0.25 volts per inch sensitivity with a frequency response within 1.5 db to 4.5 Mc. Intensity modulation may be applied to the grid of the cathode-ray tube at 60 cps internally, or an external voltage may be applied to a binding post on the front panel.

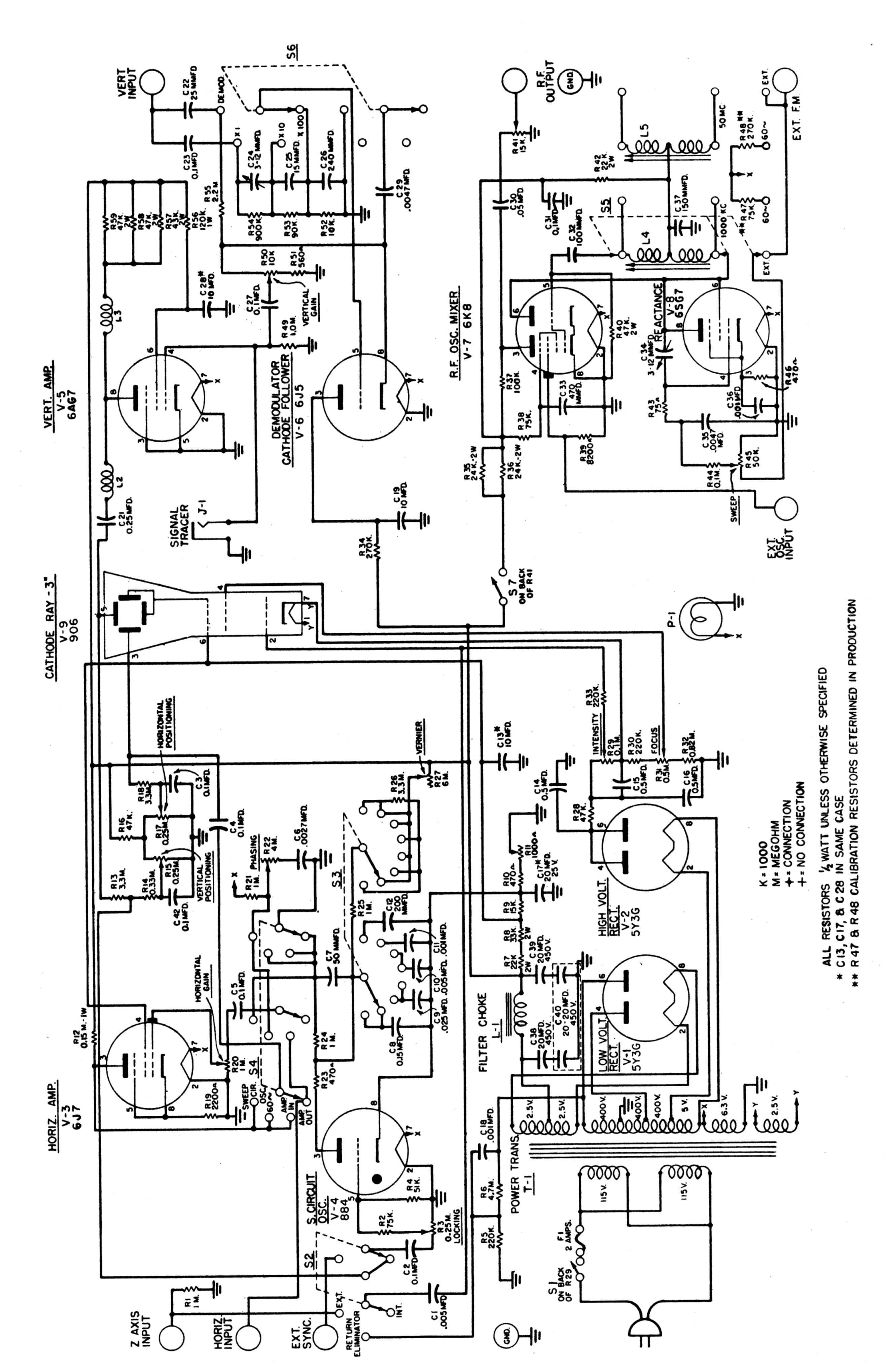

Digital File Copyright © 2018 StevenJohnson.com. This digital file provided free by Steve's Antique Technology at StevenJohnson.com and may not be resold in any form.